

Laborator 3

O introducere în limbajul VHDL

Introducere

- cel mai cunoscut și puternic limbaj de descriere hardware a circuitelor. Permite modelarea și simularea sistemelor numerice la orice nivel de complexitate.
- posibilități ale programului:
 - descompunere ierarhică a sistemelor
 - descriere structurală a sistemelor
 - descriere comportamentală a sistemelor
 - permite verificarea funcțională a sistemului prin simulare
 - permite verificare temporală a sistemului
 - permite dezvoltarea unui proiect în echipă
 - independent de tehnologie și proces de fabricație
 - portabilitate
 - suport CAD-CAE
 - disponibilitate publică
- o componentă hardware (poartă logică sau microprocesor, de exemplu) este reprezentată de un cuplu format dintr-o **entitate** și o **arhitectură** asociată. Entitatea definește conexiunile cu exteriorul, denumite porturi, prin listarea numelor, a direcției datelor și a tipului de date pentru fiecare port, iar arhitectura conține o descriere a structurii componentei, sau a comportamentului acesteia.

Un exemplu simplu

 


Fig. 12.1 *Schema logică a unei structuri combinaționale*

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;

entity FUNC is
end;

architecture VAR1 of FUNC is

    component GATES
        port (A, B, C: in STD_LOGIC;
              F: out STD_LOGIC);
    end component;

    signal A, B, C, F: STD_LOGIC;

    begin

        A <= '0', '1' after 100 NS, '0' after 300 NS;
        B <= '0', '1' after 200 NS, '0' after 400 NS;
        C <= '1', '0' after 350 NS;
        F <= not((A and B) or (not C));

        M: GATES port map (A, B, C, F);

    end VAR1;
```

Fig. 12.2 *Codul VHDL pentru descrierea comportamentală și simularea circuitului din figura 12.1*

- simularea se poate face în regim continuu sau în pași, dar în acest model nu s-au luat în considerare timpii de propagare prin porți.

- codul din figura 12.3 oferă o **descriere structurală** a circuitului, la nivel de componente și interconexiuni. Fiecare poartă logică este introdusă prin directiva *component*, se declară semnalele de intrare/ieșire A, B, C, F, dar și semnalele interne S1 și S2 (vezi figura 12.1). Se precizează apoi variația semnalelor de intrare, iar semnalele de intrare/ieșire pentru fiecare componentă de circuit sunt *mapate* pe intrările/ieșirile fiecărei componente, conform schemei electrice a circuitului.

```

architecture VAR2 of FUNC is

    component and2gate
        port (A, B: in STD_LOGIC;
              F: out STD_LOGIC);
    end component;

    component invgate
        port (A: in STD_LOGIC;
              F: out STD_LOGIC);
    end component;

    component nor2gate
        port (A, B: in STD_LOGIC;
              F: out STD_LOGIC);
    end component;

    signal A, B, C, F: STD_LOGIC;
    signal S1, S2: STD_LOGIC;

    begin

        A <= '0', '1' after 100 NS, '0' after 300 NS;
        B <= '0', '1' after 200 NS, '0' after 400 NS;
        C <= '1', '0' after 350 NS;

        p1: and2gate port map(A, B, S1);
        p2: invgate port map(C, S2);
        p3: nor2gate port map(S1, S2, F);

    end VAR2;

```

Fig. 12.3 O altă descriere VHDL pentru circuitul din figura 12.1

12.3 Descrierea VHDL a unui automat finit

 


Fig. 12.4 *Semnalele interfeței calculator-microcalculator*

 


Fig. 12.5 *Organigrama interfeței*

```

library IEEE;
use IEEE.std_logic_1164.all;

entity interfata is
    port(CLOCK, START, READY, TR, CYEND: in std_logic;
          ATTENTION, INACTIVE, CYCLE, FE: out std_logic);
end interfata;

architecture automat_finit of interfata is
    type state_type is (A, B, C, D, E, F);
    signal state: state_type;
    begin
        process(CLOCK)
        begin
            if CLOCK'event and CLOCK = '1' then
                case state is
                    when A =>
                        if (START = '1') then
                            state <= B;
                        else
                            state <= A;
                        end if;
                    when B =>
                        if (READY = '1') then
                            state <= C;
                        else
                            state <= B;
                        end if;
                    when C =>
                        state <= D;
                    when D =>
                        if (TR = '1') then
                            state <= E;
                        else
                            state <= A;
                        end if;
                    when E =>
                        if (CYEND = '1') then
                            state <= F;
                        else
                            state <= E;
                        end if;
                    when F =>
                        state <= D;
                end case;
            end if;
        end process;

        ATTENTION <= '1' when (state = B) else '0';
        INACTIVE <= '1' when (state = C) else '0';
        CYCLE <= '1' when (state = E) else '0';
        FE <= '1' when (state = F) else '0';
    end automat_finit;

```